



Amplifier is an electronic device. The device which increases the value of a signal is called amplifier. In input a weak signal is applied, in output a strong, same shape signal is gained. Amplify means to increase the value of something.

Buffer amplifier is a circuit which transforms electrical impedance from one circuit to another. The main purpose of a buffer is to prevent the loading of a preceding circuit by the succeeding one.

The equalizer stage of an amplifier allows control of the frequency working interval.

The gain stage of an amplifier raises the sound, making it better to be heard.

A single stage amplifier amplifies a weak signal but uses only a single transistor to achieve this.

Multistage Amplifiers: In practice, we need amplifier which can amplify a signal from a very weak source such as a microphone, to a level which is suitable for the operation of another transducer such as loudspeaker . This is achieved by cascading number of amplifier stages, known as multistage amplifier

The role of capacitor in amplifier

Coupling Capacitors: A coupling capacitor is a capacitor which is used to couple or link together only the AC signal from one circuit element to another. The capacitor blocks the DC signal from entering the second element and, thus, only passes the AC signal.

Bypass Capacitor: A bypass capacitor is a capacitor that shorts AC signals to ground, so that any AC noise that may be present on a DC signal is removed, producing a much cleaner and pure DC signal.

A bypass capacitor essentially bypasses AC noise that may be on a DC signal, filtering out the AC, so that a clean, pure DC signal goes through without any AC ripple.

Differences between MOSFET, JFET and BJT

- BJT is current control device. While FET and MOSFET's are voltage control device
- BJT is bipolar junction device while FET and MOSFET's are junction transistor devices.
- BJT has lower input impedance while FET and MOSFET's are high input impedance device.
- BJT is not thermally stable but FET and MOSFET's are thermally stable due to increase in collector current and I_{CBO} .
- BJT is more power consumption and in FET, FET has more power consumption but MOSFET's are lower power consumption device therefore MOSFET'S are preferred over than FET.

• Application BJT: for Lower current application FET : lower voltage application


MOSFET: Since power consumption is lessl therefore used in CMOS circuits.

- In the case of BJT, there are Active, saturation and cutt -off mode.
- in the case of FET, ohmic and pinch off region
- in case of MOSFET, linear and saturation region.
- FET is easily damage but BJT is robust.
- FET is faster than BJT • FET has low voltage gain while BJT has high voltage gain

2. Give brief information about the transistor


I choose BJT as 2n222a and JFET as a bf245a .Because cheap and enable our application. Also I investigate and I saw the same application on the internet.also I put the datasheet .

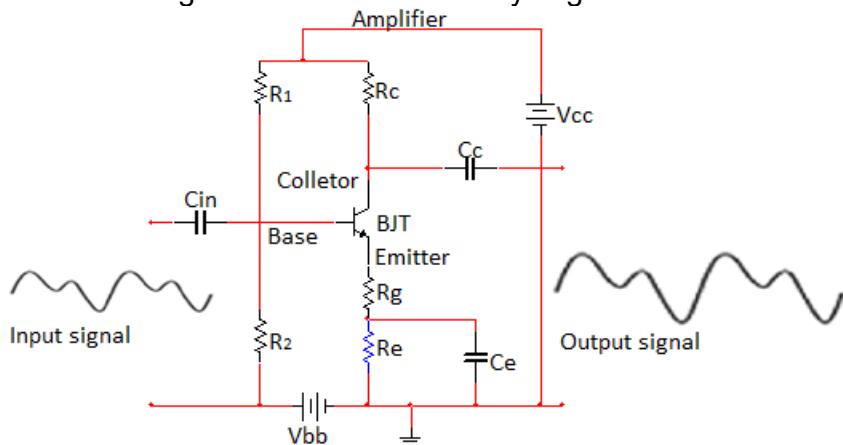3. Design a single stage audio amplifier with parameters given by your laboratory assistants (frequency, gain). Discuss about the design (is it possible or not? If not, why?). Yes we can design .But the noise will very high.




Common Emitter Transistor Amplifier Circuit

I put one design

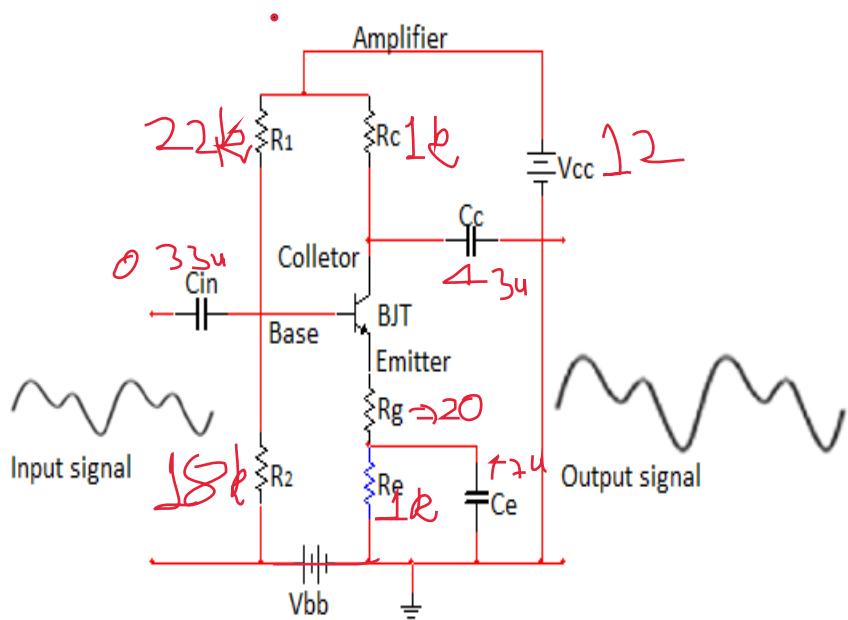


we can design this circuit i give the pdf


4-

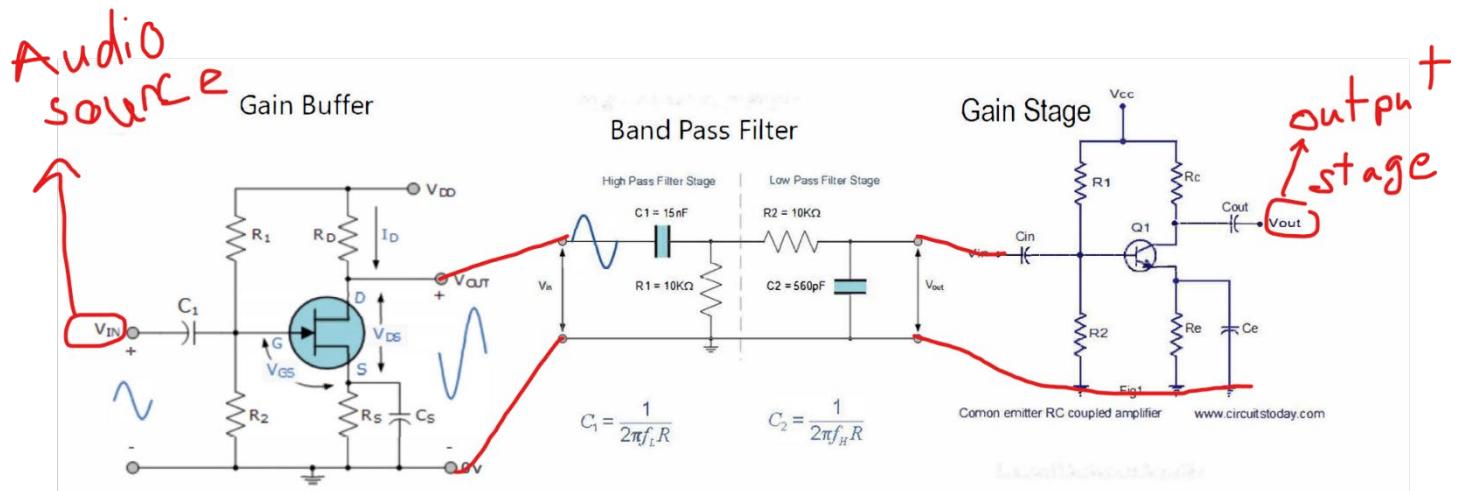

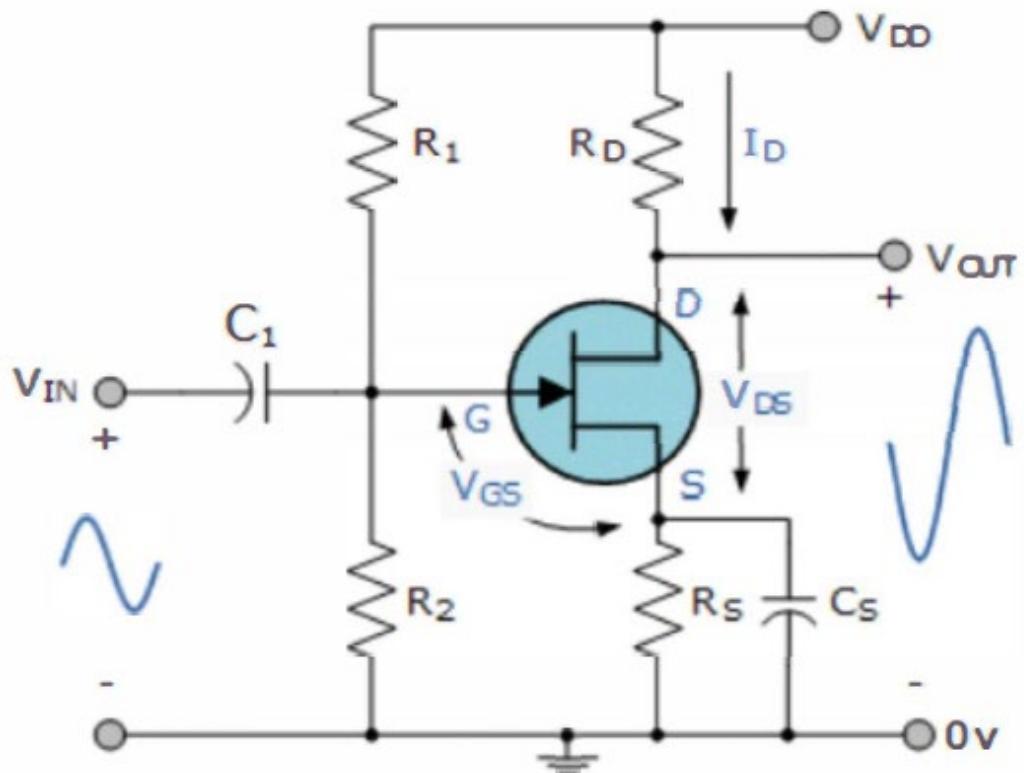DESIGN PART Buffer Stage: BF245A =>>>YOU CAN LOOK DATASHEET



Buffer stage

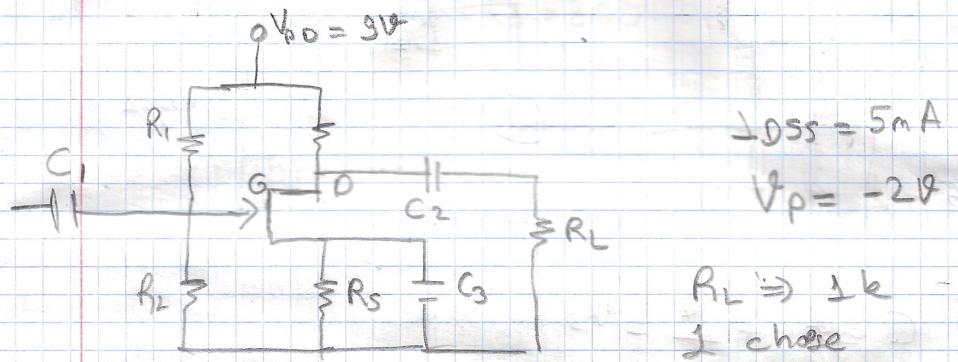


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= 5 \times 10^{-3} \left(1 + \frac{V_{GS}}{\frac{V_P}{2}} \right)^2$$

$$I_D = 5 \times 10^{-3} \left(\frac{V_{GS}^2}{4} + V_{GS} + 1 \right)$$

S SAC equivalent model

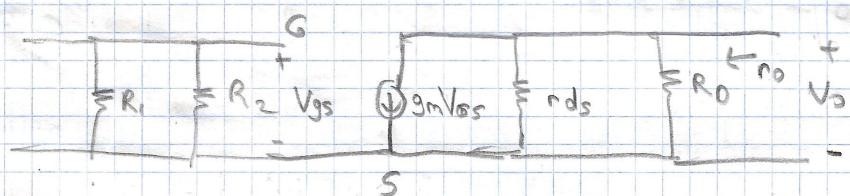

$$\Delta V = -g_m (R_o \parallel r_{ds} \parallel R_L)$$

$$\text{if } r_{ds} \geq 10R_o \quad \Delta V \Rightarrow -g_m (R_o \parallel R_L)$$

Here I choose V_s as 0.9 for Q point

stabilization and $R_s = 300$ so $I_D = \frac{0.9}{300}$

$$I_D = 3 \text{ mA}$$

$$V_G = \frac{R_2}{R_1 + R_2} \cdot V_{DD} \quad I_D = 3 \text{ mA} = 5 \times 10^{-3} \left(\frac{V_{GS}^2}{4} + V_{GS} + 1 \right)$$

$$\text{and } V_{GS} \geq -2 \text{ V}$$

By doing calculation $V_{GS} = -0.45 \text{ V}$

$$V_G = V_{GS} + V_s \quad \text{where } V_s = 0.3 \text{ V}$$

$$\text{so } V_g = 0.3 - 0.45 = 0.45 \text{ V}$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_G}{V_{DD}} = \frac{0.45}{9} = \frac{1}{20} \quad \text{so I choose } R_2 = 1k \text{ and } R_1 = 19k$$

$$g_m = \frac{2 I_{DSS}}{|V_p|} \sqrt{\frac{I_D}{I_{DSS}}} \Rightarrow \frac{2 \times 5 \times 10^{-3}}{2} \sqrt{\frac{3}{5}}$$

$$g_m = 3.873 \times 10^{-3}$$

we can ignore r_{ds} due to $r_{ds} \geq 10k\Omega$

$$G_m \Rightarrow 1 = \underbrace{-g_m}_{X} \underbrace{R_o || R_L}_{1} \Rightarrow R_L = 1k\Omega$$

$$R_o || R_L = \frac{1}{g_m} \Rightarrow \frac{1}{3.873 \times 10^{-3}} = 258.2$$

$$R_o || R_L = 258.2 \quad \text{by calculating } R_o = 287 \Omega$$

$$V_{DS} = V_{DD} - I_D (R_s + R_o)$$


$$\Rightarrow 9 - 3 \times 10^{-3} (287 + 300)$$

$$V_{DS} \Rightarrow 7.24$$

we apply the values on the circuit

DESIGN PART BANDPASS FILTER


Band Pass Filter

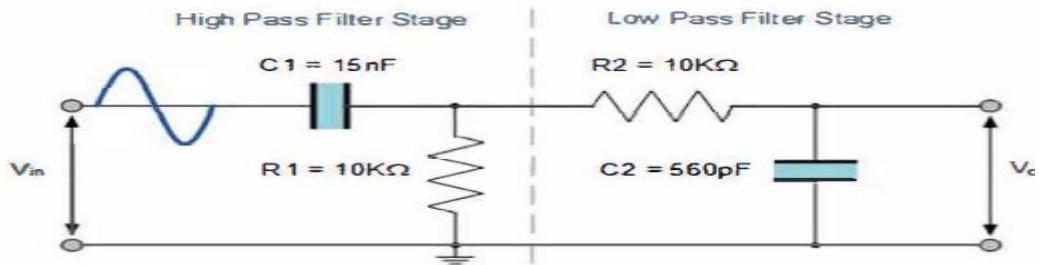

$$C_1 = \frac{1}{2\pi f_L R}$$

$$C_2 = \frac{1}{2\pi f_H R}$$

bandpass filter

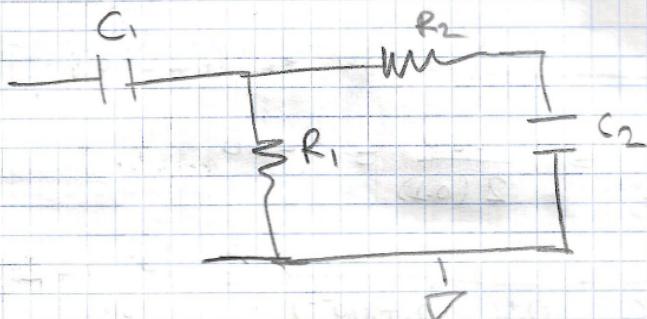

$$C_1 = \frac{1}{2\pi f_L R}$$

$$f_L \Rightarrow 340$$

$$R_1 \Rightarrow 100 k$$

if we write $C_1 \Rightarrow 4.68 n \Rightarrow 4.7 n$

$$C_2 = \frac{1}{2\pi f_H R}$$


$$f_H = 16.6 k$$

$$R_2 \Rightarrow 100 k$$

$$C_2 \Rightarrow 96 p \Rightarrow 100 p$$


we apply the values on the circuit

DESIGN PART 3-GAIN STAGE

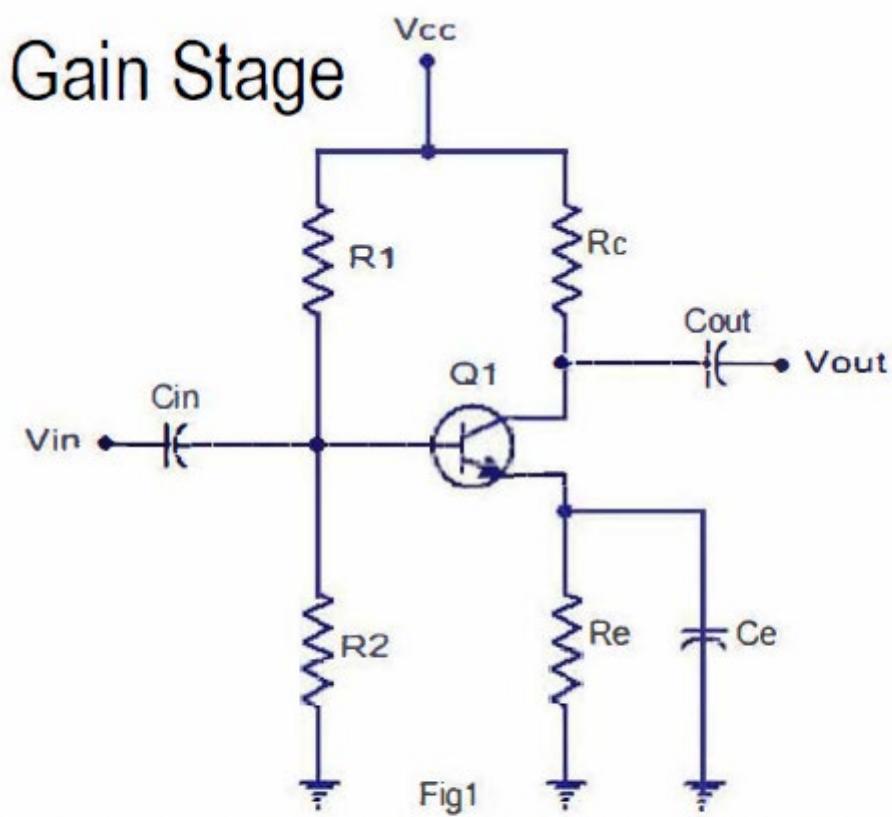

Common emitter RC coupled amplifier

CALCULATION

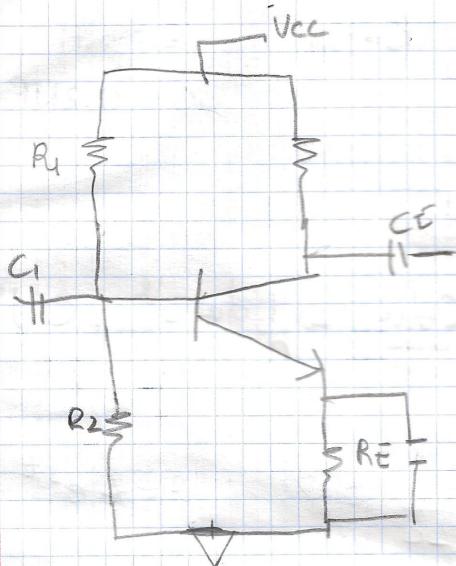

$$\begin{aligned}\beta &= 200 \\ r_e &= 0.02 \text{ mA} \\ I_c &= 4 \text{ mA}\end{aligned}$$

$$V_{CE} = 4 \text{ V}$$

$$r_e = \frac{26 \text{ mV}}{4 \text{ mA}} = 6.5 \Omega$$

$$Av = \frac{R_c}{R_E + r_e} = 4 = \frac{R_c}{R_E + 6.5} = 4R_E + 26 = R_c$$

$$(V_{CC} - V_{CE}) = (R_E + R_C) I_C$$

$$(9 - 4) = (R_E + 4R_E + 26) \text{ mA}$$

$$5 = (5R_E + 26) \cdot 4 \text{ mA}$$

$$12.50 - 26 = 5R_E \quad R_E = 244.8 \Omega$$

$$R_C = 1005.2 \Omega$$

$$R_{B2} \leq \frac{\beta \cdot R_E}{10} \quad R_B \leq \frac{200 \cdot 245}{10} \quad R_{B2} \leq 4.9 \text{ k}\Omega$$

$$R_{B2} \Rightarrow 4 \text{ k}\Omega$$

$$V_b \Rightarrow V_{be} + I_C R_E$$

$$V_b = 0.7 + 4(244.8) \Rightarrow 1.68$$


$$\frac{1.68}{9} = \frac{R_2}{R_1 + R_2} \Rightarrow \begin{aligned}R_1 &\Rightarrow 4.35 R_2 \\ R_1 &\Rightarrow 4.35 \times 4 \text{ k}\Omega \\ R_1 &\Rightarrow 17.42 \text{ k}\Omega\end{aligned}$$

we apply the values on the circuit

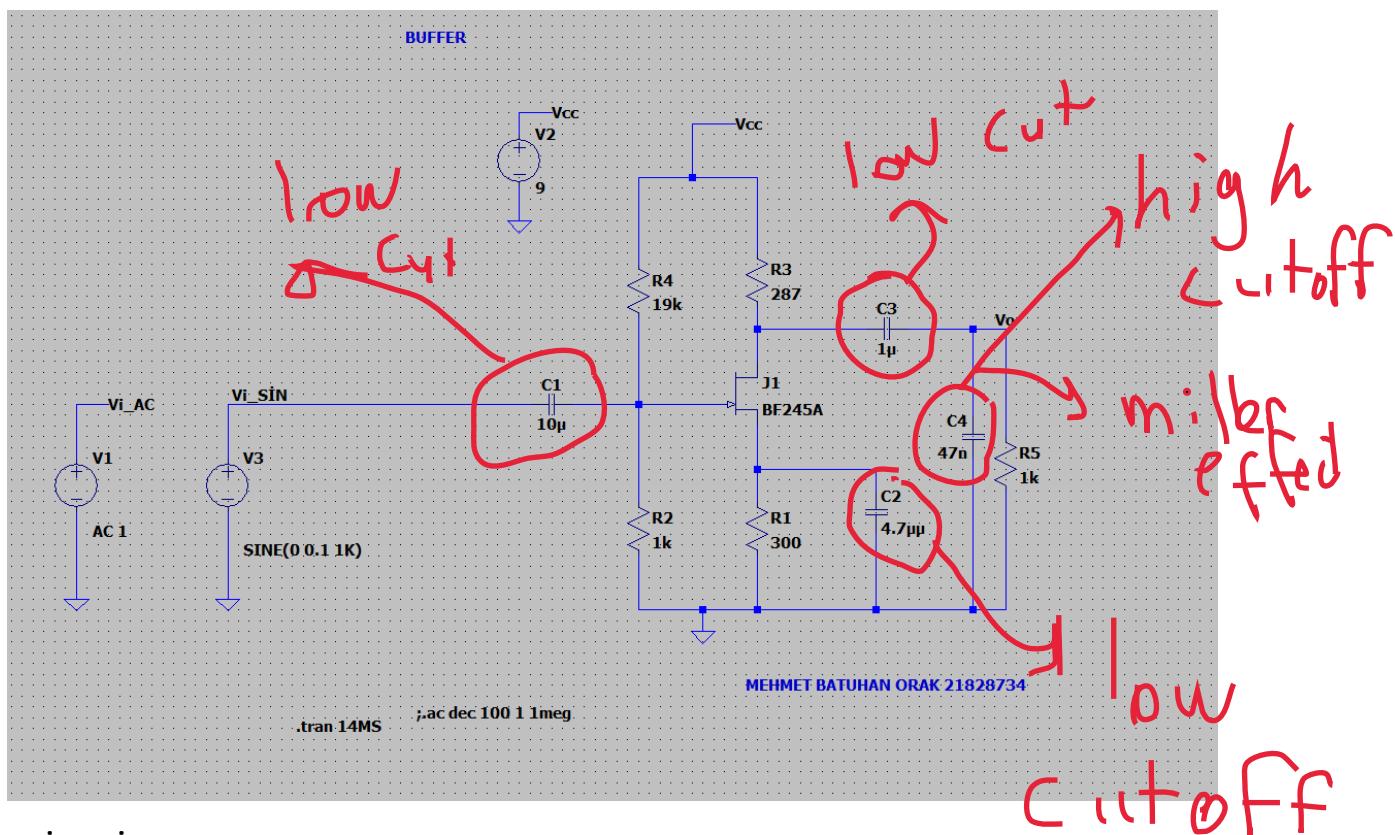PART 2: SIMULATION


Buffer Stage:

I CHOOSE THE CAPACITORS WITH TRYİNG MY WORKİNG AREA




WE CAN SEE AMPLITUDE IS THE SAME AND GAIN -1


FREQUENCY WORKING AREA

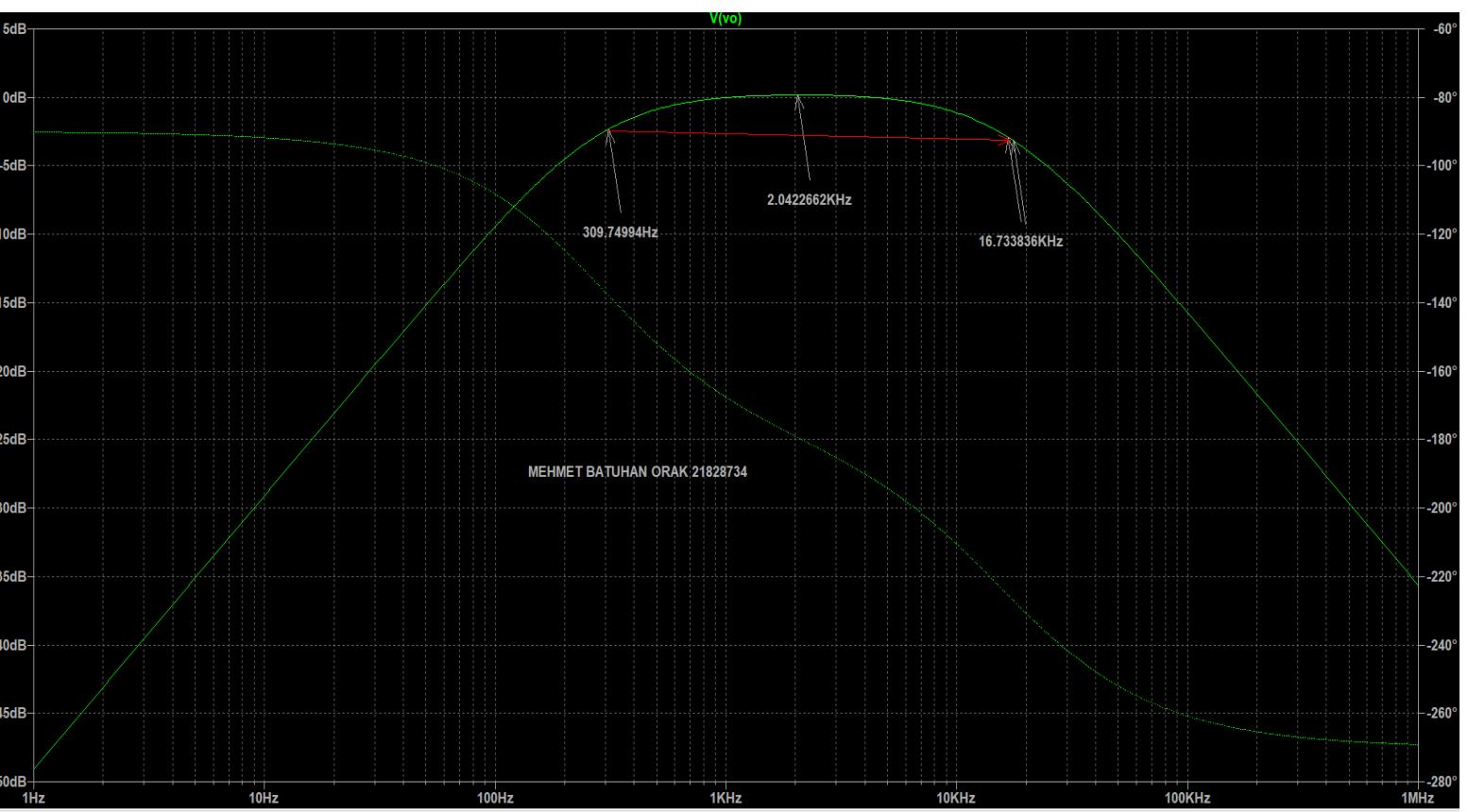

2-BANDPASS FILTER:

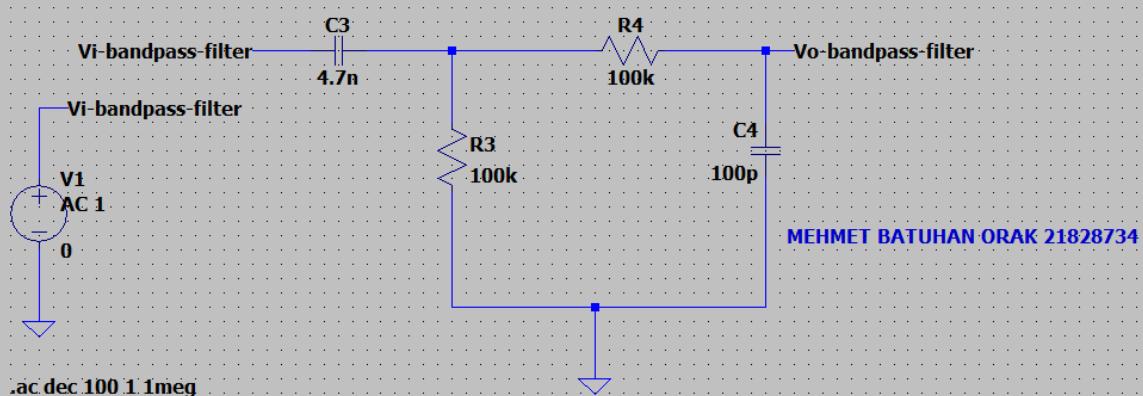


FREQUENCY WORKING AREA

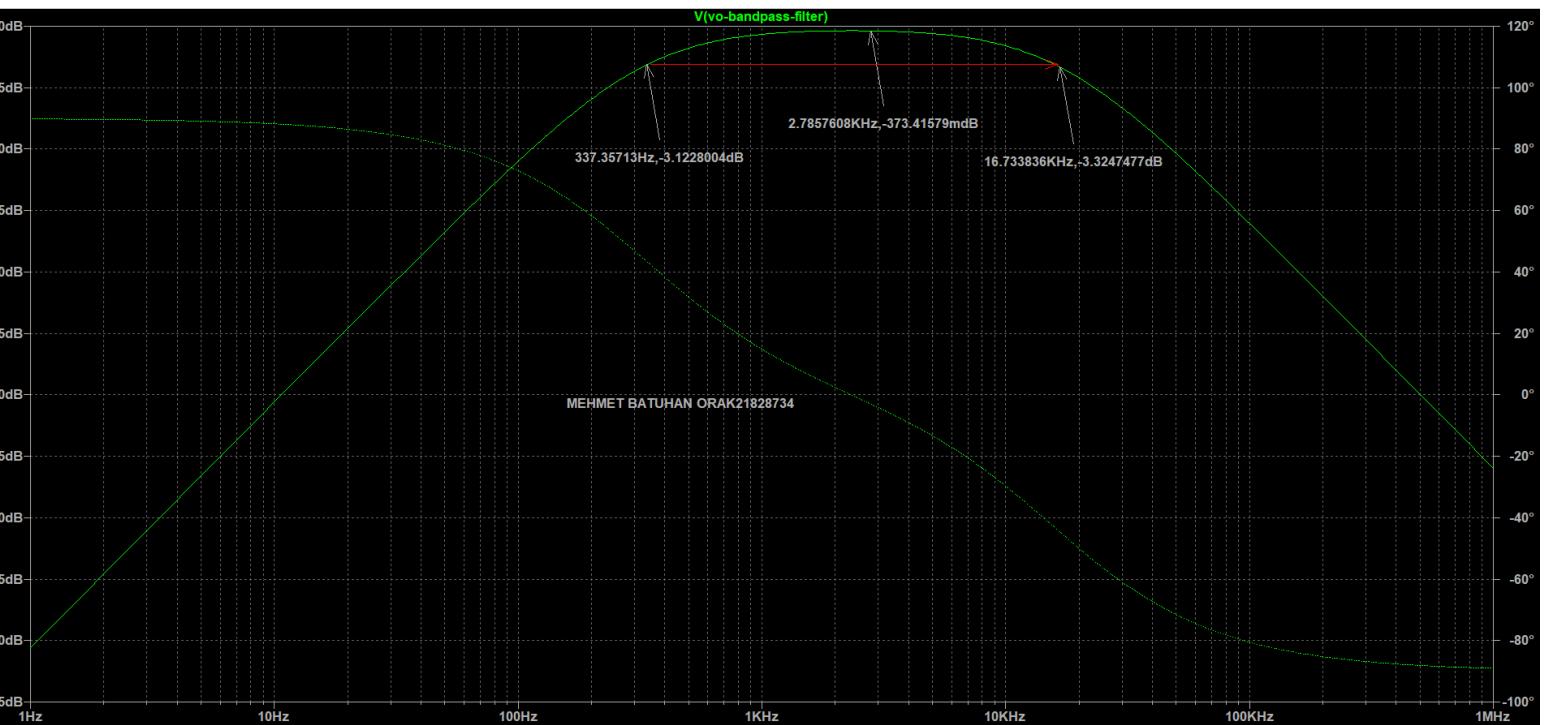


MY FREQUENCY AREA =>>>340-16.600

3-GAIN STAGE

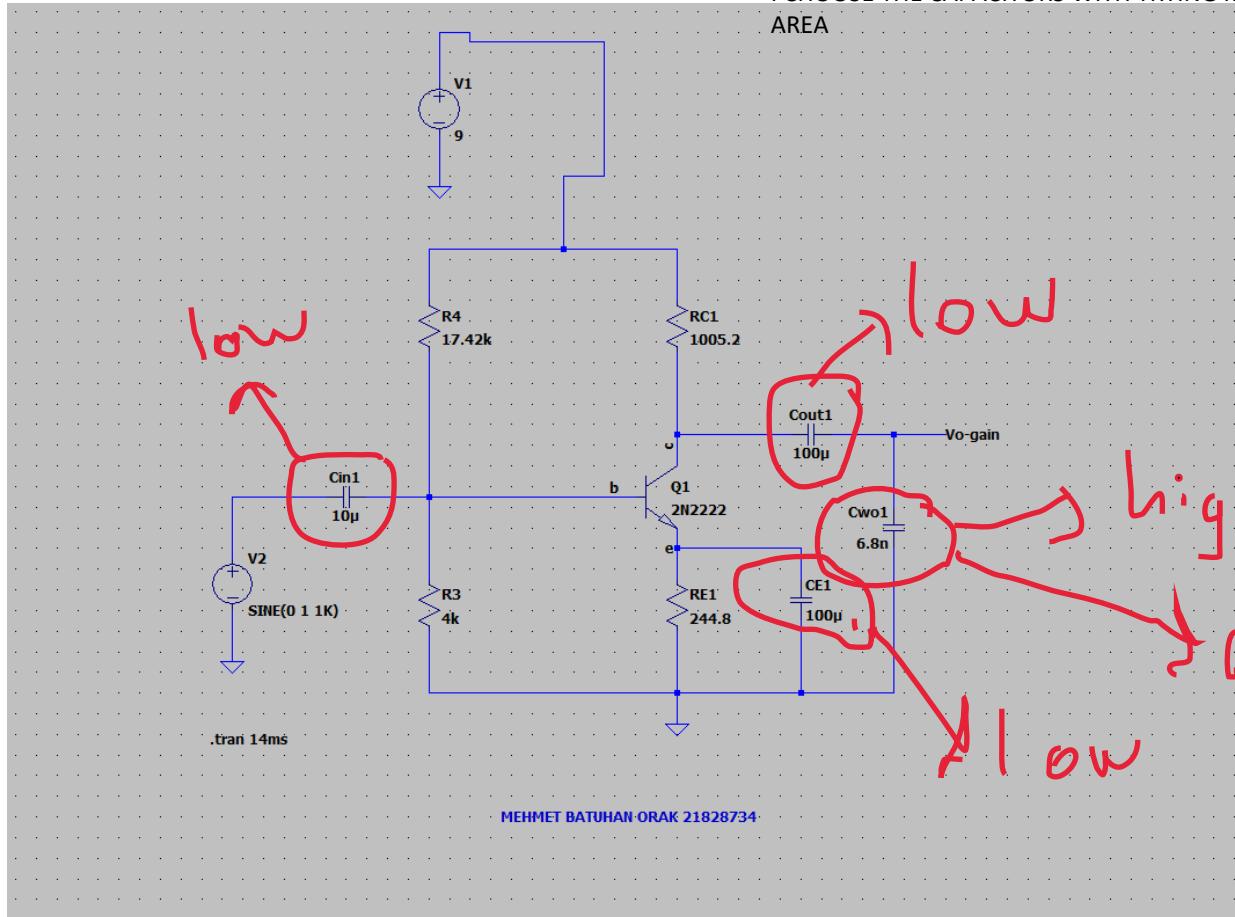


I CHOOSE THE CAPACITORS WITH TRYİNG MY WORKİNG AREA

MY GAIN WAS =4 AND THIS THE GRAPH

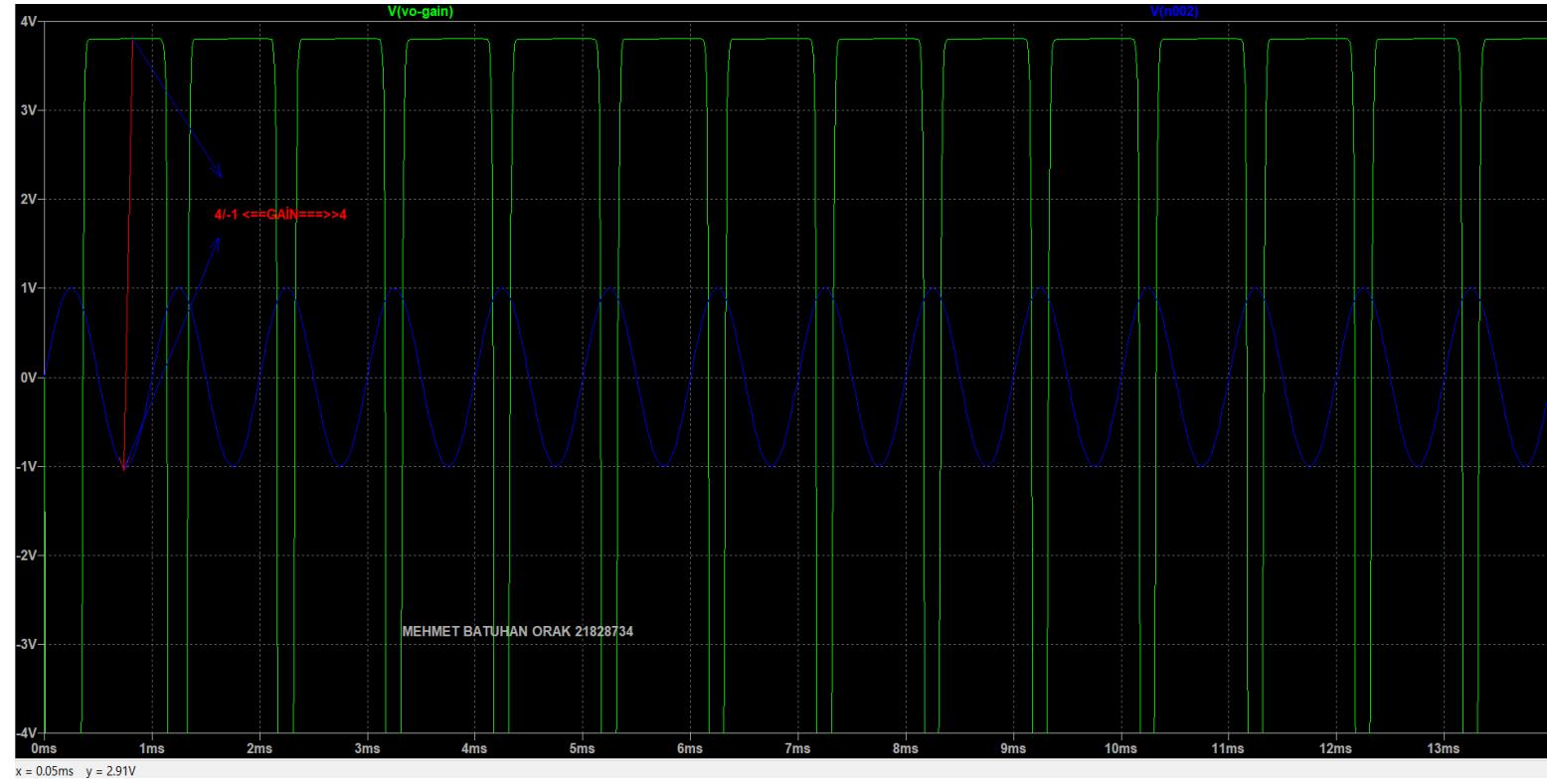


FREQUENCY WORKING AREA

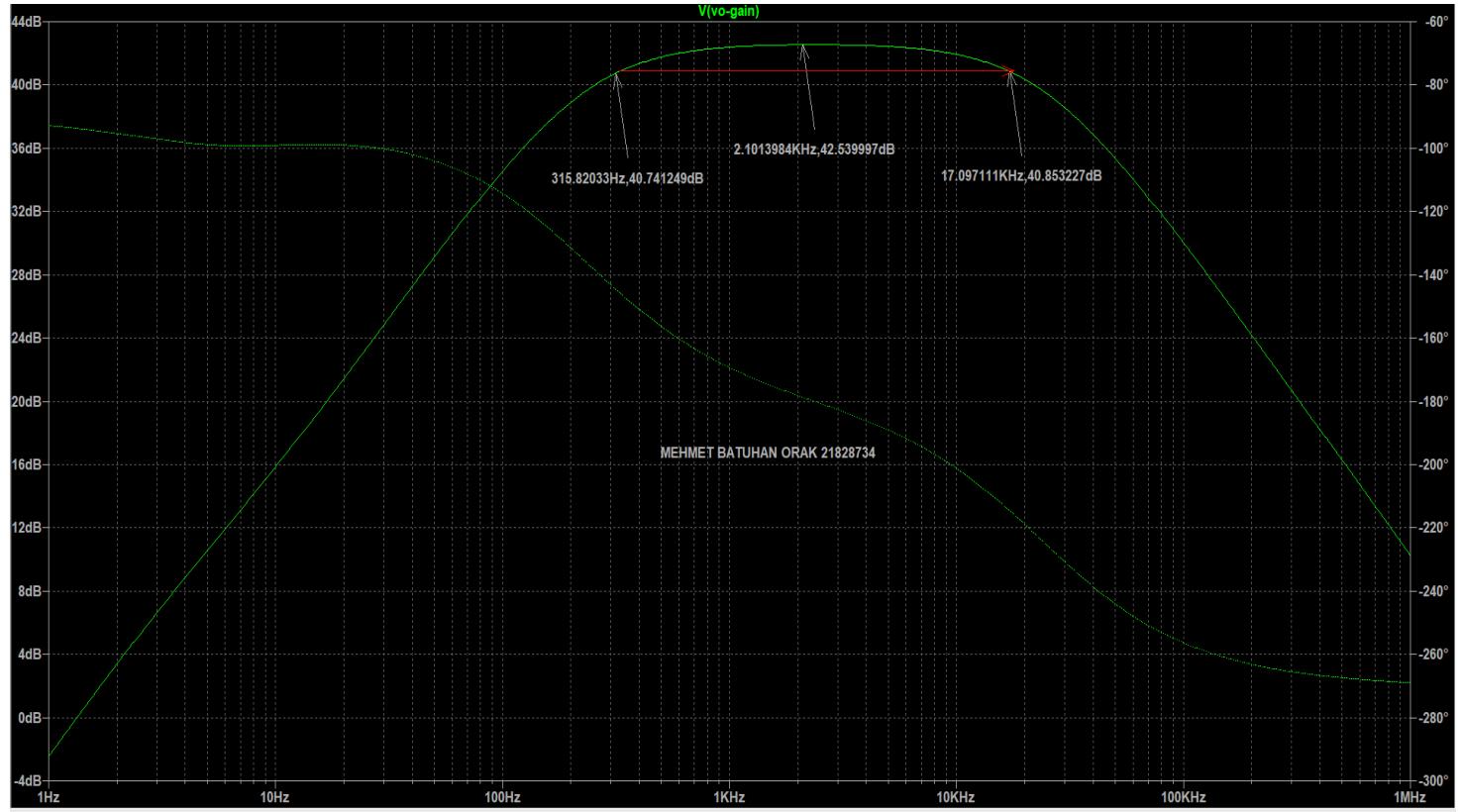


MY FREQUENCY AREA =>>>340-16.600


4- PROJE

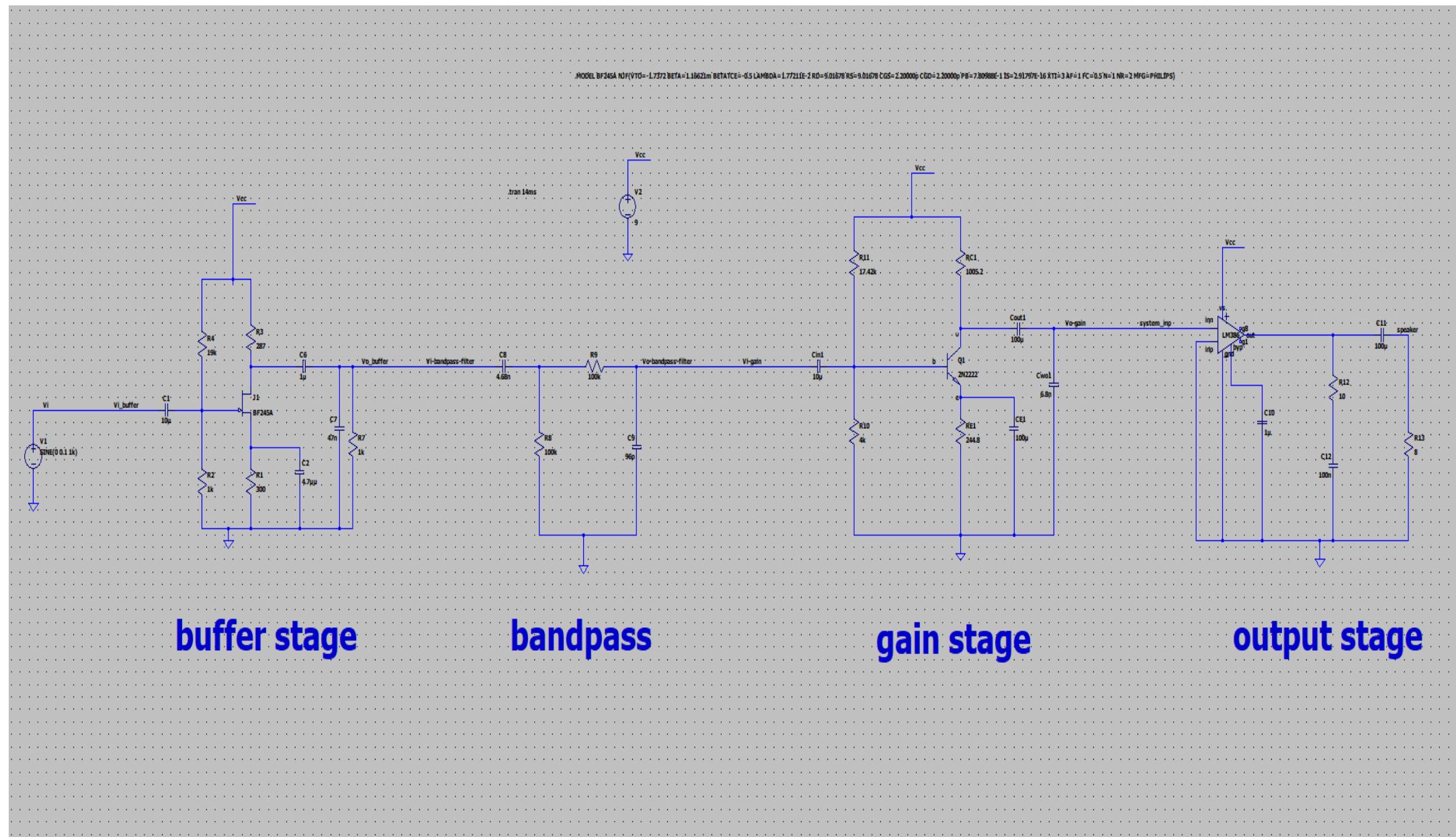

4-PROJE SIGNALS

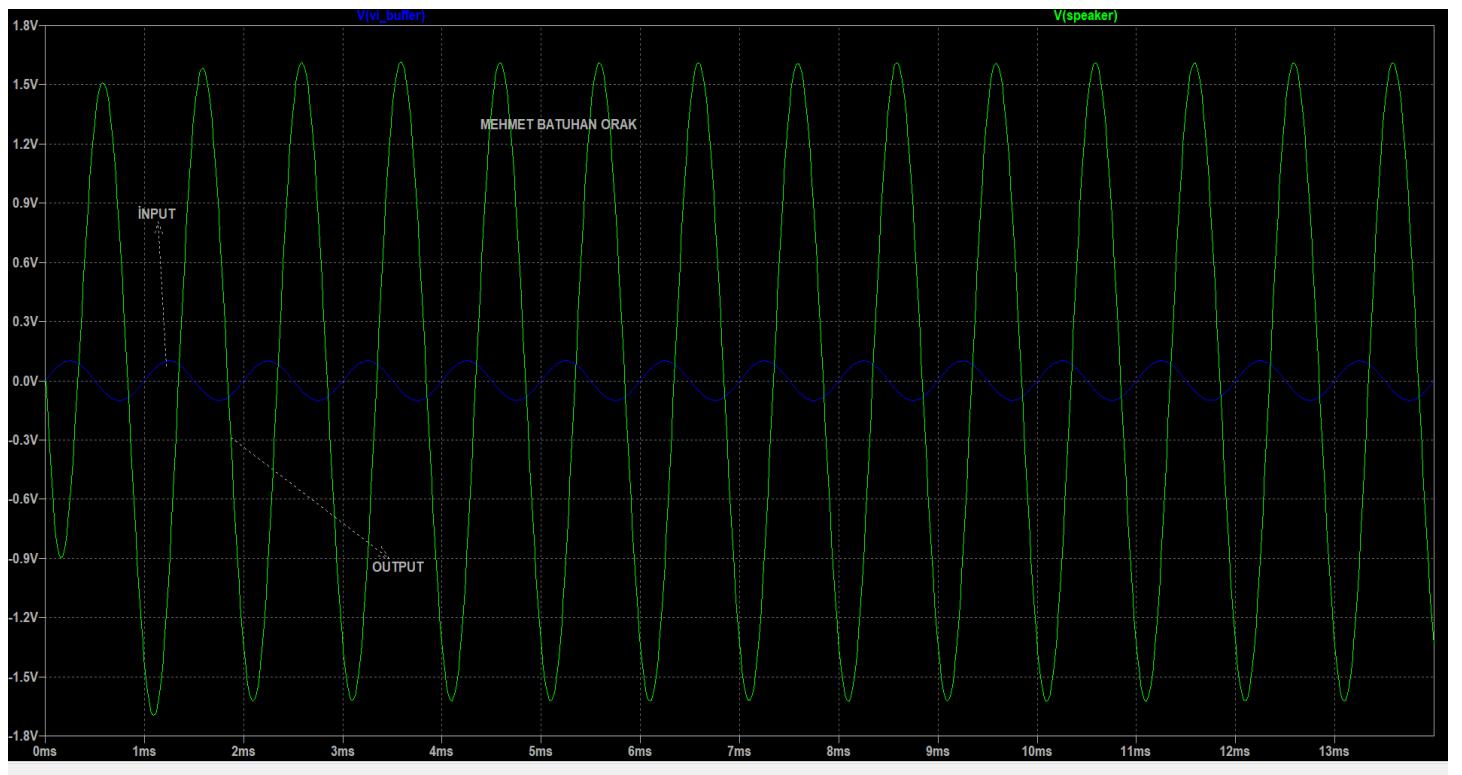

FREQUENCY WORKİNG AREA

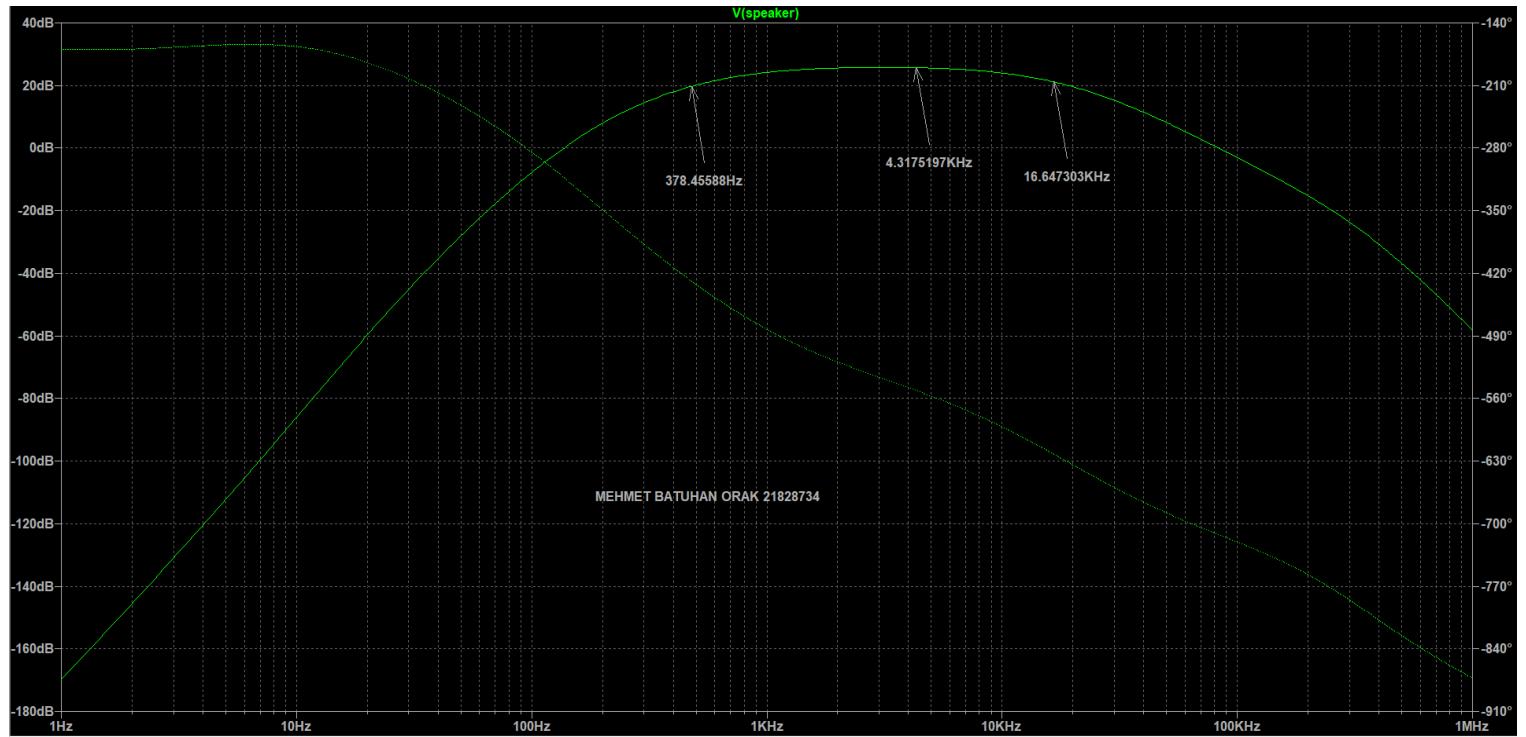

MY FREQUENCY AREA =>>>340-16.600